

### Transistor-Level Circuit Design

For each expression below, create a switch level implementation using NFETs and PFETs. Here you **can** assume you have the complements of each input. Your design should contain no shorts or floats. Use as few transistors as you can, but do not simplify the expression.

$$Out = B(A + C)$$

$$Out = \overline{A}B + C$$

$$Out = A \oplus B$$

$$Out = \overline{A}\overline{B}(\overline{C} + D)$$

$$Out = \overline{A}(\overline{B} + (CD))$$

$$Out = \overline{A}B + \overline{C}D$$

$$Out = \overline{A}(\overline{B} + \overline{C})$$

$$Out = \overline{A}(\overline{B}C + \overline{D})$$

$$Out = \overline{A}(B + \overline{C}(\overline{D} + F))$$

$$Out_1 = A\overline{B} + \overline{A}B\overline{C}$$

$$Out_2 = \overline{A}(B\overline{C} + \overline{D}E)$$

$$Out_3 = \overline{\overline{A}B + C + \overline{D}E}$$