

Decoders

Implement a two to four decoder with enable using only basic gates (AND, OR, NAND, NOR, and NOT). Assume that you have the input signals and their complements. Be sure to label the inputs IN_0 , IN_1 , and $Enable$, and the outputs OUT_3 , OUT_2 , OUT_1 , and OUT_0 .