

Divide by 60 Counter

In the course of designing a sixty second counter, you have elected to design a cascable divide by six counter.

Part A Design a toggle cell using basic gates and transparent latch devices (do not implement the transparent latches). Inputs should be *CountEnable* and \overline{Clear} . The output is *Out*.

Part B Now use this device (in icon form) to build a divide by six counter that does not cause problems at 50 seconds. Inputs should be *CountEnable* and *ExternalClear*. Outputs should be *Out₀*, *Out₁*, *Out₂* and *MaxCount* which goes high when the output is at its maximum count.