

## Registers and Latches

**Part A** Implement a transparent latch using only four 2-input NAND gates and one inverter. Label *in*, *out*, and *enable* signals. Use correct mixed logic notation.

**Part B** Implement a **register with write enable**, using only transparent latches, NAND, NOR, AND, OR, and NOT gates. Use mixed logic design methodology. You do **not** have to implement transparent latches from basic gates. Label input and output signals *INPUT*, *WE*, *Phi1*, *Phi2*, and *OUTPUT*. Label the output of the first latch as *X*.

**Part C** Now complete the timing diagram for this register based on the specified inputs. Point *X* is defined as the output of the first latch in the register. *OUTPUT* is the output of the register. Assume all internal storage is initially zero. Ignore gate propagation delay.

