Toggle Cell Components

Part A

IN	C	Out
\overline{A}	0	0
\overline{A}	1	A

IN	C	Out
\overline{A}	0	A
\overline{A}	1	\overline{A}

IN	C	Out
\overline{A}	0	Q_o
\overline{A}	1	A

Part B

