

### Priority Encoders

**Part A** Complete the following truth table for a priority encoder. Assume the priority order (from highest to lowest) is  $IN_2, IN_0, IN_3, IN_1$ .

$IN_3$	$IN_2$	$IN_1$	$IN_0$	$OUT_1$	$OUT_0$	$Valid$
0	0	0	0	X	X	0
X	0	X	1	0	0	1
0	0	1	0	0	1	1
X	1	X	X	1	0	1
1	0	X	0	1	1	1

**Part B** Implement the following priority encoder using basic gates (AND, OR, NAND, NOR, and NOT). Label all inputs and outputs.

$IN_3$	$IN_2$	$IN_1$	$IN_0$	$OUT_1$	$OUT_0$	$Valid$
0	0	0	0	X	X	0
X	X	X	1	0	0	1
X	X	1	0	0	1	1
X	1	0	0	1	0	1
1	0	0	0	1	1	1

