

A client wants you to design the logic for a device to control a forced-air furnace.

- The logic will have three inputs:
 - hot – this input will be active ('1') if the furnace is too hot.
 - door – this input will be active if the furnace door is open.
 - fuel – this input will be active when fuel is present.
- The logic will have two outputs.
 - blow – turns on the blower fan when active.
 - Should not be active if the door is open, if there is no fuel, or if the furnace is too hot.
 - Otherwise, should be active.
 - alert – sounds an alarm to let someone know that something is wrong.
 - Should be active in two situations: 1) when the furnace is out of fuel, and 2) when the door is open and the furnace is too hot.
 - Otherwise, should be inactive.

Use the description above to write two Boolean expressions – one for each output.