

Derive the Boolean expression for the following CMOS circuit:

