

Draw a gate diagram (a gate-level schematic) that directly implements the Boolean expression below. Do not manipulate the expression. Use only standard, symmetrical gates (NOT, AND, OR, NAND, NOR). Gates may have as many inputs as desired.

$$OUT = A + \overline{\overline{B \cdot \overline{C + D}}} + (C + D) \cdot E$$