

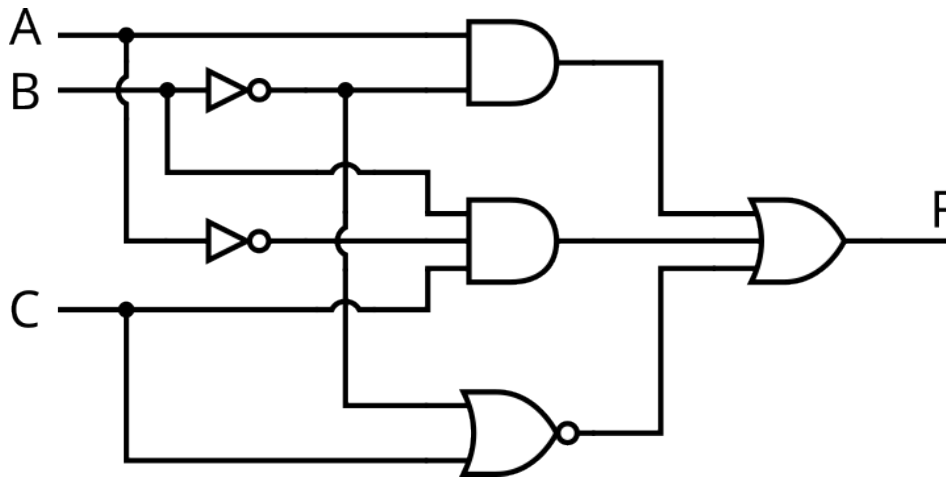


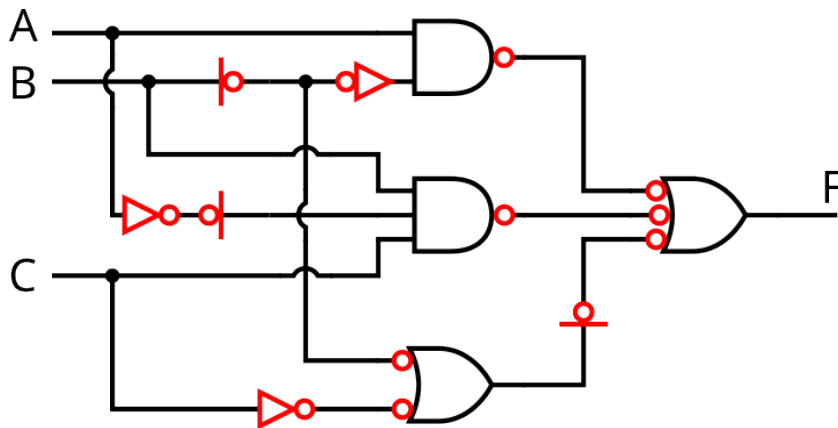a) Write the Boolean expression that the following gate schematic implements.



$$F = A \cdot \bar{B} + \bar{A} \cdot B \cdot C + \bar{\bar{B} + C}$$

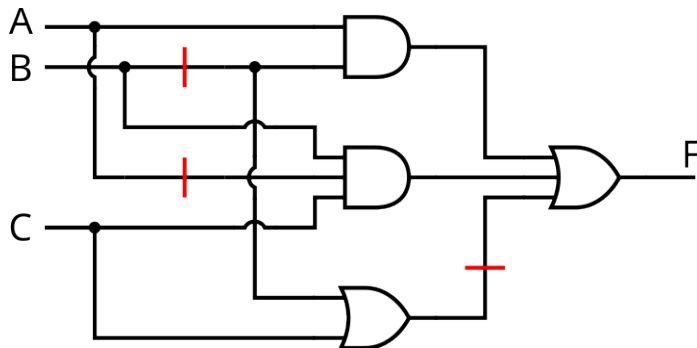b) Starting with the expression above, draw a starting point for mixed-logic schematic manipulation, then perform a manipulation to create an implementation that uses only NAND gates and inverters.



c) How many inverters does the result of b) require?

Three