



Complete the timing simulation below for nodes B, C, and D in the circuit above using the timing parameters $T_{\text{PNOT}}=3$ ns and $T_{\text{PAND}}=5$ ns. Include annotations for the time of each transition, as is done on signal A. There is room at the bottom for additional nodes if desired.

