 


Consider the circuit below with input X and output Z. Note that the nodes labeled 'Q' are internal to the system (they are not inputs or outputs). Timing parameters for the components are listed in the table.



T _p NAND	10ns
T _p ADDER	100ns
T _p DFF	20ns
T _{su} DFF	5ns
T _h DFF	2ns

a)
Assume that a rising clock edge occurs at time t=0. At what times does input X need to be stable?

b)
Assume that a rising clock edge occurs at time t=0. At what time do you expect the output to be correct?

c)
What is the maximum frequency at which the flip-flops can be clocked and the circuit still behave as intended? Leave your answer as a mathematical expression in terms of the given timing parameters.

d)
Assume that the adder is a ripple-carry adder (where the carry for each lower place value feeds into the next place value). As you increase the frequency of the clock *just* to the point where the circuit stops behaving as intended, which flip-flop's value would you expect to be incorrect?